

# CS 21 Project 1: Bulls and Cows Circuit Simulation

Department of Computer Science  
College of Engineering  
University of the Philippines - Diliman

## 1 Introduction

For this project, you are to create a *Logisim* circuit simulation of the *Bulls and Cows* game.

### 1.1 Bulls and Cows

*Bulls and Cows* is a logic game wherein the player has to guess a predetermined number in at most some number of attempts. For each guess made, the player is given the number of *bulls* and *cows* of the guess as a clue.

A digit of the guess can be classified as being a bull, a cow, or neither. A *bull* is a digit of the guess  $G$  that is present in the answer  $A$  and is found in the same position in both  $G$  and  $A$ . A *cow* is a digit of  $G$  found in  $A$  but is found in different positions in  $G$  and  $A$ .

As a four-digit example,  $A = 1234$  and  $G = 2034$  has 2 bulls (digits 3 and 4 of  $G$  are in the right positions) and 1 cow (digit 2 of  $G$  is in the wrong position)—note that the digit 0 of  $G$  is not in  $A$ , so it is neither a bull nor a cow.

### 1.2 Logisim

Logisim<sup>1</sup> is a free and open-source digital logic circuit simulator. The simulator is written in Java (which allows it to be cross-platform) and produces OS-agnostic output files (`.circ`).

## 2 Project Specifications

Create a Logisim circuit simulation of the Bulls and Cows game implemented as described in the subsections below.

### 2.1 Circuit labels

For the **main circuit**, text corresponding to the names and class numbers of each group member must be visible (and the group name if it exists).

Define  $C$  to be a set  $C_0, C_1, \dots, C_{G-1}$  containing the class numbers of each of the  $G$  group members sorted in ascending order (i.e.,  $C_0$  is the smallest class number in the

---

<sup>1</sup><http://www.cburch.com/logisim/>

group).  $N$  is defined as follows:

$$N = \sum_{i=0}^{G-1} 51^i C_i$$

For **all** other user-defined **subcircuits**, a small textbox with content equal to  $N$  must be present in the lower-right-hand corner when at **50% zoom level**.

**A 5% deduction will be incurred for noncompliance or incorrect execution of any of the above.**

## 2.2 Input/output components

All input and output components must be in the *main circuit*—**the circuit is not valid otherwise and will not be eligible for checking**.

### 2.2.1 Input components

The circuit must have at least the following input components:

- Numpad (one button for each number from 0 to 9 labeled accordingly)
- Left/Up button (labeled < or ^)
- Right/Down button (labeled > or v)
- Enter button (labeled x)

### 2.2.2 Output components

The circuit must have at least the following output components:

- 7-segment LEDs (8 in total)
  - Displayed four-digit number; one for each digit
  - **Bulls** (labeled)
  - **Cows** (labeled)
  - **Lives** (labeled)
  - **Wins** (labeled)
- LEDs (9 in total)
  - Digit selector for four-digit number; one for each digit (position beside each digit accordingly)
  - **Start** LED (labeled)
  - **Game** LED (labeled)
  - **Wait** LED (labeled)
  - **Win** LED (labeled)
  - **Lose** LED (labeled)

## 2.3 Phases

The circuit should have the following phases with behavior defined in the succeeding subsections:

1. Setup Phase
2. Wait Phase 1
3. Wait Phase 2
4. Guess Phase
5. Compute Phase
6. Done Phase
7. Hold Phase
8. Reset Phase

### 2.3.1 Setup Phase

During this phase, the user can enter the four-digit answer. Only one digit may be selected at any given time; this is shown using one of the four indicator LEDs beside each 7-segment LED representing the digits. Pressing the directional buttons while on a triggering edge changes the selected digit exactly once; the selector LEDs must simultaneously reflect the change as well. Only the selected digit must be modified by a numpad key press.

Once the digits of the intended answer are set, the **Enter** button may be continuously pressed until the next triggering edge to transition into **Wait Phase 1**.

Note that among the LEDs, only the selector LEDs and the **Start** LED are active. For the 7-segment LEDs, only the **Bulls**, **Cows**, and **Lives** are inactive.

### 2.3.2 Wait Phase 1

During this phase, all display components are inactive except the **Wins** display and both the **Wait** and **Start** LEDs. A transition into **Wait Phase 2** occurs automatically after the next triggering edge.

### 2.3.3 Wait Phase 2

During this phase, all display components except both the **Wins** display and the **Setup** LED (note that the **Wait** LED is inactive as well). A transition into the **Guess Phase** occurs automatically after the next triggering edge.

### 2.3.4 Guess Phase

During this phase, the player can input digits in a manner similar to how input is done during the **Setup Phase** (this implies that the selection LEDs and relevant 7-segment LEDs are active). The **Game** LED along with the **Bulls**, **Cows**, **Lives**, and **Wins** 7-segment LEDs must all be active.

Once the digits of the intended guess are set, the **Enter** button may be continuously pressed until the next triggering edge to transition into the **Compute Phase**.

### 2.3.5 Compute Phase

During this phase, all display components are inactive except the **Wins** display and both the **Game** and **Wait** LEDs.

If the player has either guessed the number correctly (win) or has **zero** lives left after an incorrect guess (lose), a transition into the **Done Phase** occurs automatically after the next triggering edge. Otherwise, an automatic transition back into the **Guess Phase** occurs during the said edge.

Note that once the transition into the **Guess Phase** is complete, the value shown in the **Lives** display must have been decremented by one to reflect that an attempt has been made. The **Bulls** and **Cows** display should be updated according to their definitions.

### 2.3.6 Done Phase

During this phase, only the **Lives**, **Wins**, and four-digit number displays are active along with either the **Win** or **Lose** LEDs reflecting proper game state.

Note that the four-digit display must show the correct answer. The **Lives** display should show its previous value decremented by one to reflect that an attempt has been made. The value shown in the **Wins** display must be incremented by one if the player has won during this round.

The **Enter** button may be continuously pressed until the next triggering edge to transition into the **Hold Phase**.

### 2.3.7 Hold Phase

During this phase, all display component states are the same as with the **Done Phase** with the exception of the **Wait** LED being active as well.

If the **Enter** button is pressed during the next triggering edge, a transition into the **Reset Phase** occurs. Otherwise, a transition back into the **Done Phase** occurs. In practice, this means that the **Enter** button must be held for **two** triggering edges to transition from the **Done Phase** into the **Reset Phase**.

### 2.3.8 Reset Phase

During this phase, only the **Lives** display is active. An automatic transition back into the **Setup Phase** occurs after the next triggering edge. This phase serves as a pause which separates the current round from the next.

## 2.4 Input/output behavior

### 2.4.1 Input behavior

- All buttons are expected to be pressed for at least one clock cycle
- Buttons must be activated **exactly once** per user-defined triggering edge
- Holding a button continuously for two clock cycles must register as two button presses
- Only one button is pressed at any given point in time

	<b>S</b>	<b>W1</b>	<b>W2</b>	<b>G</b>	<b>C</b>	<b>D</b>	<b>H</b>	<b>R</b>
4-digit number	✓			✓		✓	✓	
Bulls				✓				
Cows				✓				
Lives				✓		✓	✓	
Wins	✓	✓	✓	✓	✓	✓	✓	✓
Digit selectors	✓*			✓*				
Start LED	✓	✓	✓					
Game LED				✓	✓			
Wait LED		✓			✓		✓	
Win LED						✓*	✓*	
Lose LED						✓*	✓*	

Table 1: I/O active state matrix (\* indicates certain conditions have to be met)

### 2.4.2 Output behavior

A matrix showing which components must be active during which phases is given in Table 1 for your convenience (inactive 7-segment LEDs must be blank). Listed below are details specific to each component.

- 7-segment LEDs for four-digit number
  - Shows *answer digits* during the **Setup Phase**, **Done Phase**, and **Hold Phase**
  - Shows *guess digits* during the **Guess Phase**
- Wins 7-segment LED
  - Has 0 as its initial value during power on
  - Maximum supported value is 15 (show 10 to 15 as hex)
  - Value overflows back to 0 after exceeding 15 wins
  - Value is incremented once during the **Done Phase** if the player has won during the current round
- Lives 7-segment LED
  - Has 7 as its initial value per round
  - Value is decremented after each **Compute Phase** regardless of correctness of guess
- Bulls and Cows 7-segment LEDs
  - Proper value is updated and displayed during the **Guess Phase**
  - Duplicate digit cases need not be handled
- Win and Lose LEDs (labeled)
  - Active only if the player has won/lost during the current round
  - Player wins if the guess is equal to the answer even if the player has zero lives
  - Player loses if the guess is not equal to the answer and the player has zero lives

## 2.5 Tips

- Divide the circuit design into self-contained **subcircuits** with **well-defined input and output pins** planned beforehand (see next section for suggested subcircuits); this allows both an easier time with debugging and a way to delegate tasks
- Imported subcircuits may not be modified directly; however, you may open subcircuits in a separate Logisim window and select the **Reload Library** option on the main circuit after the subcircuit edits have been saved
- Subcircuit display symbols may be manually edited via the **Edit Circuit Appearance** which allows changing of the component shape, reordering of I/O ports, and adding of on-screen labels
- Go through at least the first four sections of Logisim’s **User Guide/documentation** and the **Library Reference**; the sections **Subcircuits** and **Wire bundles** are must-reads before laying out your circuit design
- You will likely use all the gates in the **Plexers library**—ensure that you know what each component does and what other components are available in Logisim
- You may need to use tri-state buffers (**Controlled Buffer/Inverter** in Logisim) for better I/O control
- Make extensive use of Logisim’s **Wire Bundle**, **Splitter**, and **Data Bits** features to save space—it is of note that the model solution has 19 well-defined subcircuits
- Logisim allows both **negating gate inputs** to avoid adding separate inverters and **resizing gate symbols** to save space and make your design cleaner
- Use **read-only memory (ROM) components** to quickly form combinational circuits from truth tables instead of deriving expressions via K-maps and mapping out logic gates
- Simple combinational logic manipulating the clock signal inputs of each flip-flop/register (i.e., **allowing/preventing flip-flop value changes based on state**) may be needed
- **Manually driving the clock** via the **Simulate > Tick Once** feature (use the shortcut!) may help with debugging
- You may use third-party libraries such as <https://github.com/marceloboeira/logisim-7-segment-display-driver>; use **floating values** (displayed as blue lines) as inputs to the said decoder to have 7-segment LEDs appear blank
- Start early, save often, and make backups (using version control systems such as *Git* is a good habit to form); no special consideration will be given to make up for accidental file erasures and the like

## 2.6 Subcircuit suggestions

- **Game state controller** – takes in the current state and user inputs and provides the next state as output lines (ideally derived via sequential design techniques)
- **Display controller** – has output lines directly connected to output components; input lines are processed/filtered via gate logic (multiplexers, decoders, etc.) depending on the game state

- **Memory unit** – contains most/all the flip-flops/registers of the circuit with input lines providing new values for each and output lines supplying current values to other circuits; this allows centralized management of data changes and tracking
- **Input controller** – takes in button states as inputs and converts them into logical values (e.g., which register will receive the current numpad input); this decouples how input is retrieved from the user and what values are expected by the other subcircuits (i.e., you may have a simple number input interface at first and refactor it as a numpad cleanly later on)
- **Game logic controller** – performs all computations needed during game proper (e.g., bulls/cows/lives/wins computation, win/lose signalling)

## 3 Grading

### 3.1 Extra credit

Two opportunities are given to earn at most **30 bonus points** with details given below. Note that bonus points will only be granted if the cumulative score without bonuses amount to **at least 60%**.

#### 3.1.1 Generate random answer

Add an extra button labeled **R** that, when continuously pressed during the next triggering edge, randomizes the current input for the answer during the **Setup Phase** once. Note that this button must **not** be functional for any other phase. The new value must be displayed immediately after the triggering edge. Holding the button for multiple triggering edges should result in a new number after each triggering edge.

The four-digit value must **not** have any repeating digits and must be generated with an *acceptable level of randomness* (consult your instructor if you have questions regarding this definition).

You are allowed to use the **Random Generator** component of Logisim. A seed value of 21140145 with 16 data bits **must** be used **without skipping any valid number generated in the sequence**—no credit will be given otherwise.

Proper implementation of the said extension will merit **15 bonus points**.

#### 3.1.2 User input validation

The project specifications allows players to input answers and/or guesses with duplicate digits; the implementation is not required to handle numbers with duplicate digits. A logical extension to the project is to disallow inputs leading to duplicate digits.

Add an extra LED labeled **E** (for *error*) which should activate while the user is pressing down on a numpad button which will result in a number with duplicate digits. Note that this LED should only activate during either the **Setup Phase** or the **Guess Phase** (phases allowing digit input).

Finally, the default value for the answer that is set during the **Setup Phase** of each round should be 1234. The default guess set during the first **Guess Phase** of each

round should be 9876.

Proper implementation of the said extension will merit **15 bonus points**.

### 3.2 Scoring rubric

Criterion	Points
Ten-key numpad provides input as expected	10
Selector buttons and LEDs are correct with respect to digit input	5
<b>Enter</b> button works as expected	5
<b>Start</b> , <b>Game</b> , and <b>Wait</b> are activated during the right phases	5
All non-selector LEDs are activated in the right sequence	5
All 7-segment LEDs are deactivated at the right instances	5
Four-digit display shows the correct values for each phase	10
Number of bulls is properly computed	5
Number of cows is properly computed	10
Number of lives is properly computed	15
Number of wins is properly computed	15
<b>Win</b> and <b>Lose</b> are activated under the proper win conditions	10
<b>Bonus 1:</b> Valid random answer button	15
<b>Bonus 2:</b> User input validation	15
	<b>130/100</b>

### 3.3 Testing

- Expect all test input values to have unique digits (i.e., no duplicate digits) unless *user input validation* has been implemented
- The clock will be running at either 2 Hz or 4 Hz
- Earned points may be withdrawn for particular items if answers to related questions are deemed insufficient or outright wrong

## 4 Submission Details

Submit an archive `cs21172project1.zip` (or `.tar.gz`) containing all relevant *Logisim circuit files* (`.circ`) through the UVLê submission module. Ensure that your archive contains **ALL** `.circ` files needed to run properly on a fresh system with Logisim (either verify this yourself or ask your instructor before the deadline to check if the submission is valid). **Projects with missing and/or corrupted files will not be checked. No leeway will be given for this.**

**Note:** non-working or late submissions will NOT be credited.

**Warning:** Logisim allows a multitude of ways to detect plagiarism; members of all groups suspected of plagiarism will be given an INC and **must** undergo a lengthy process during the **midyear break** to prove otherwise.

**All group members must be present during project checking.**



Note that project submission and checking may be done **earlier** than the specified dates below in case of scheduling concerns.

**Deadline:** 2018 May 23, 11:59pm (before Thursday)

**Project demo/checking:** 2018 May 24 (Thursday; time to be announced)